Electronic Devices & Circuits Laboratory

Experiment 1

V–I Characteristics of PN Junction & Zener Diodes,
Clipper and Clamper Circuits

Bhargav K (EE25BTECH11013)
Department of Electrical Engineering
IIT Hyderabad

Aditya Appana (EE25BTECH11004)
Department of Electrical Engineering
IIT Hyderabad

Contents

1 Aim **2**

2 Components Used **2**

3 PN Junction Diode **2**
3.1 Theory . . . 3
3.2 Circuit and Simulation (Forward Bias) . . . 3
3.3 Observation Table – Forward Bias (to be filled in lab) . . . 5
3.4 Observation Table – Reverse Bias (to be filled in lab) . . . 5

4 Zener Diode **6**
4.1 Theory . . . 6
4.2 Observations - Forward Bias (to be filled in lab) . . . 7
4.3 Circuit and Simulation - Forward Bias . . . 7
4.4 Circuit and Simulation - Reverse Bias . . . 9
4.5 Observations - Reverse Bias (to be filled in lab) . . . 11

5 Clipper Circuits **11**
5.1 Theory . . . 11
5.2 Positive Clipper (clips above +1 V) . . . 12
5.3 Negative Clipper (clips below -1 V) . . . 14
5.4 Biased (Two-Level) Clipper . . . 15
5.5 Observation Table – Clippers . . . 17

6 Clamper Circuits **17**

6.1 Theory 17
6.2 Positive Clamper 18
6.3 Negative Clamper 19
6.4 Observation Table – Clampers 19

7 Calculations / Analysis **20**

8 Results and Conclusion **20**

1 Aim

- To plot the forward and reverse V–I characteristics of a PN junction diode and find its cut-in voltage, static and dynamic resistance, and reverse saturation current.
- To plot the forward and reverse V–I characteristics of a Zener diode and find its breakdown voltage V_Z and Zener resistance R_Z.
- To design and test positive, negative and biased clipper circuits, and positive and negative clamper circuits, and record the input-output waveforms.

2 Components Used

Component	**Value/Part**	**Qty**
PN junction diode	1N4007 / 1N4148	1
Zener diode	1N4733A ($V_Z = 5.1$ V)	1
Regulated DC supply	0–30 V	1
Function generator	0–1 MHz	1
CRO / DSO	20 MHz	1
Digital multimeter	–	2
Resistors	1 kΩ, 4.7 kΩ, 10 kΩ	as needed
Capacitor	0.1 μF	1
Breadboard, wires, probes	–	as needed

3 PN Junction Diode

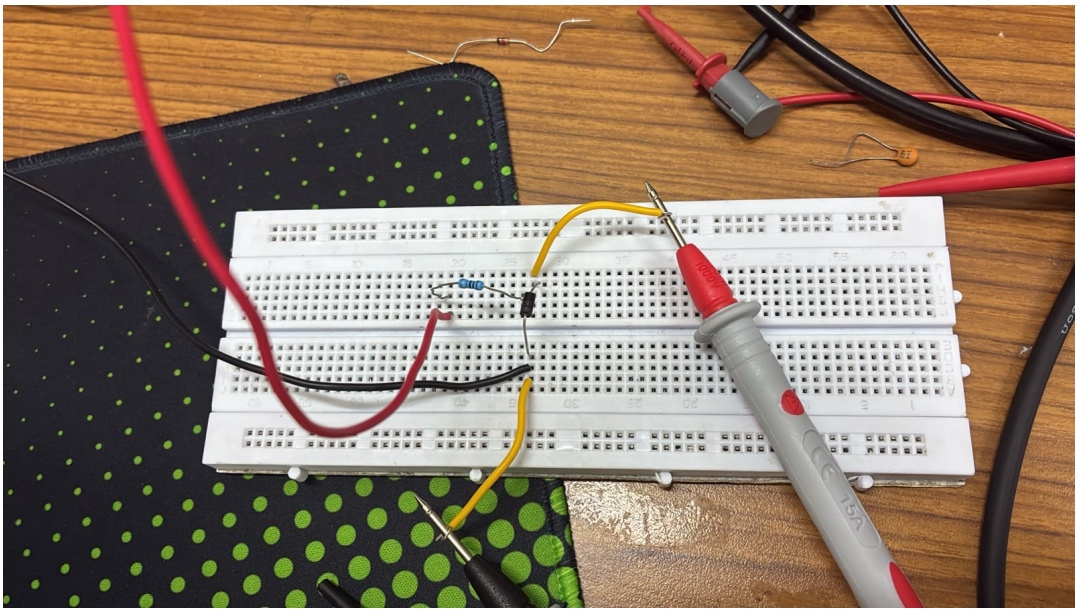


Figure 1: Forward Biased

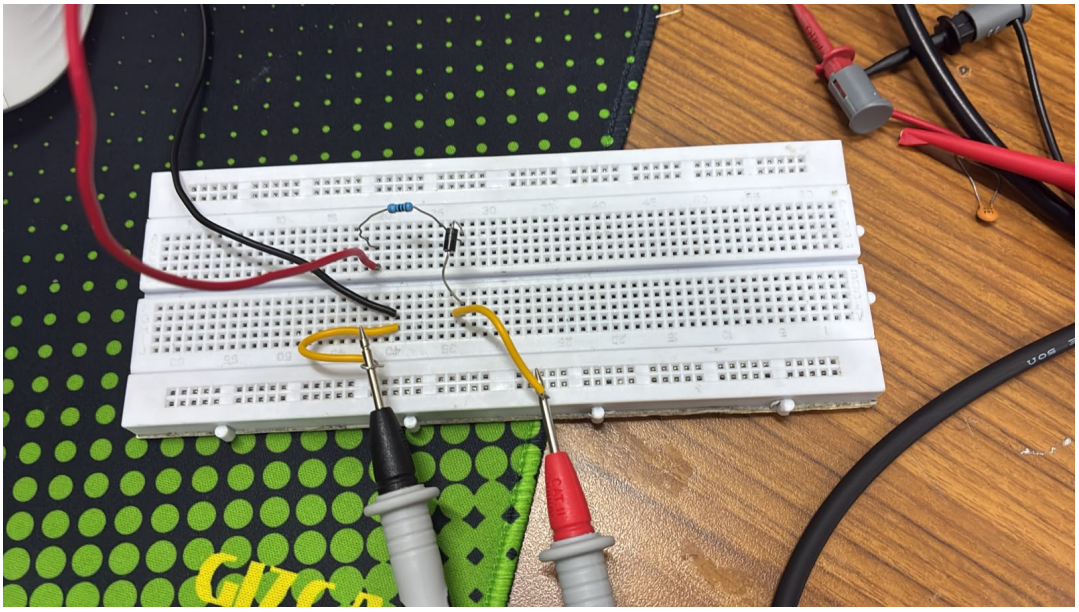


Figure 2: Reverse Biased

3.1 Theory

A PN junction diode conducts mainly in one direction. In forward bias, once the applied voltage crosses the cut-in voltage V_γ (about 0.7 V for silicon), the current starts rising very fast for a small increase in voltage, because majority carriers are being injected across the junction in large numbers. In reverse bias, only a small reverse saturation current I_0 flows due to minority carriers, and this stays almost constant until breakdown happens at a large negative voltage.

The diode current is approximately given by the diode equation:

$$I = I_0 \left(e^{V/\eta V_T} - 1 \right) \tag{1}$$

where V_T is the thermal voltage ($\approx$ 26 mV at room temperature) and η is the ideality factor.

From the forward characteristic we can find:

- **Static resistance** at a point: $R_{DC} = V/I$
- **Dynamic resistance** near a point: $R_{AC} = \Delta V/\Delta I$

3.2 Circuit and Simulation (Forward Bias)

The circuit was simulated in LTSpice with a 1 kΩ series resistor and the supply swept from 0 to 0.5 V in steps of 0.1 V, followed by finer steps near the knee.

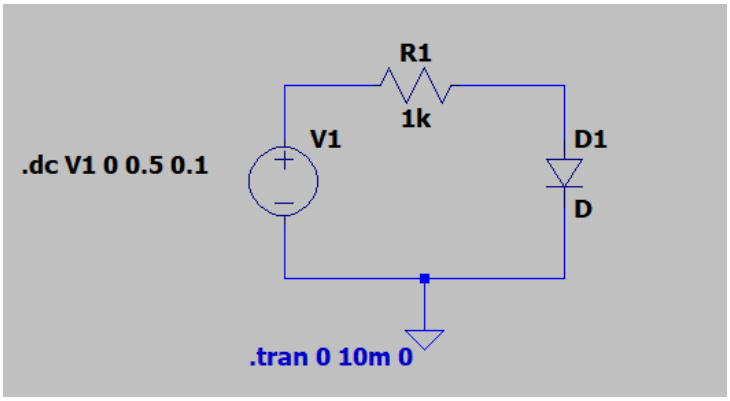


Figure 3: LTSpice circuit for PN junction diode forward bias test

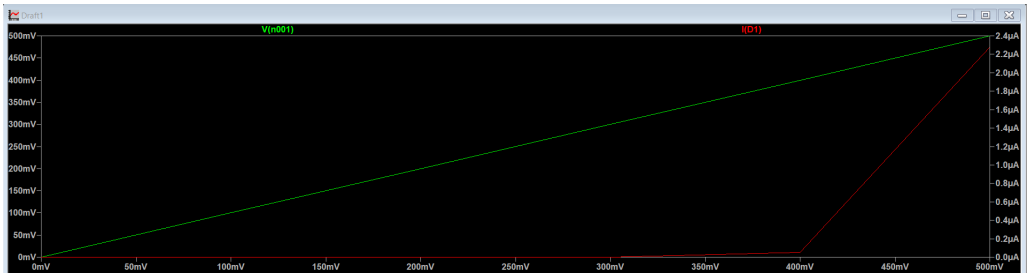


Figure 4: Simulated V–I plot: voltage across diode (green) and diode current (red) vs. sweep voltage. Current stays near zero till about 0.4 V and then rises sharply, showing the cut-in behaviour.

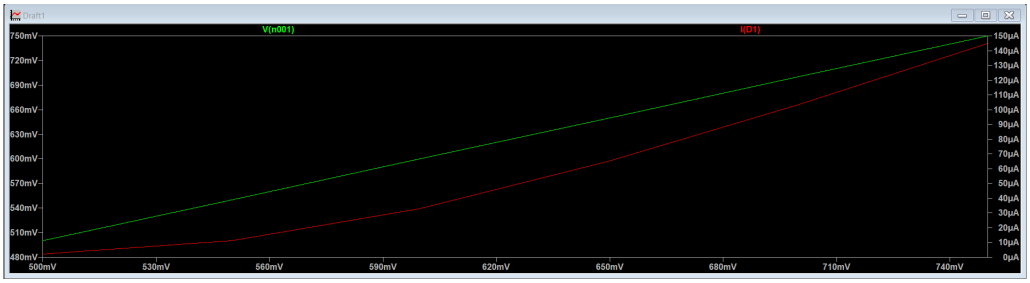


Figure 5: Simulated forward V–I characteristic, second view

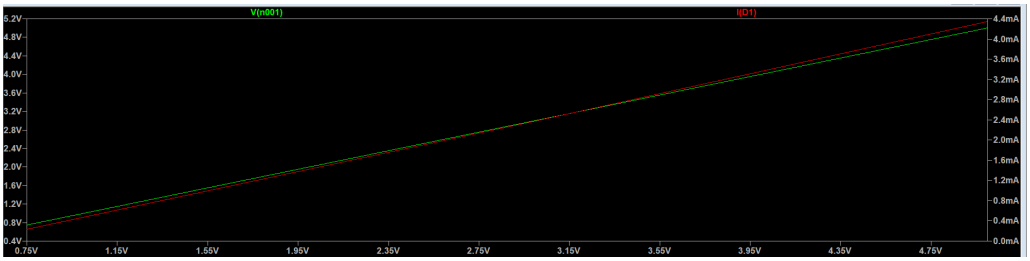


Figure 6: Simulated forward V–I characteristic, third view

From the simulation, the cut-in voltage is close to 0.4–0.5 V for the SPICE model used

(this will be verified against the measured value from the actual diode in lab, which is usually closer to 0.6–0.7 V for silicon).

3.3 Observation Table – Forward Bias (to be filled in lab)

Table 1: Forward Bias Diode Characteristics and Power Source Voltage Measurements

Diode Voltage V_f (V)	**Diode Current I_f (mA)**	**Power Source Voltage (V)**
0	0	0
0.1	0	0.1
0.2	0.0001	0.2
0.3	0.0001	0.3
0.397	0.0053	0.4
0.472	0.0384	0.5
0.496	0.0674	0.55
0.5135	0.1017	0.6
0.5266	0.139	0.65
0.537	0.1793	0.7
0.5466	0.2207	0.75
0.635	2.02	2.64
0.663	4	4.64
0.678	5.995	6.65
0.689	8	8.64
0.698	9.9994	10.62
0.706	12.02	12.61
0.7109	14.05	14.61
0.716	16.009	16.5
0.72	18.01	18.43
0.723	20	20.33

3.4 Observation Table – Reverse Bias (to be filled in lab)

No simulation was done for this part since the reverse saturation current of a real diode model is very small and not reliably captured in LTSpice's default diode model. This will be measured directly in the lab using a microammeter.

Table 2: Reverse Bias Diode Characteristics and Power Source Voltage Measurements

Diode Voltage Vf (V)	**Diode Current (mA)**	**Power Source Voltage (V)**
0	0	0
4.99	0	5
9.97	0	10
14.964	0	15
19.95	0	20
24.931	0.0001	25
29.919	0.0001	30

4 Zener Diode

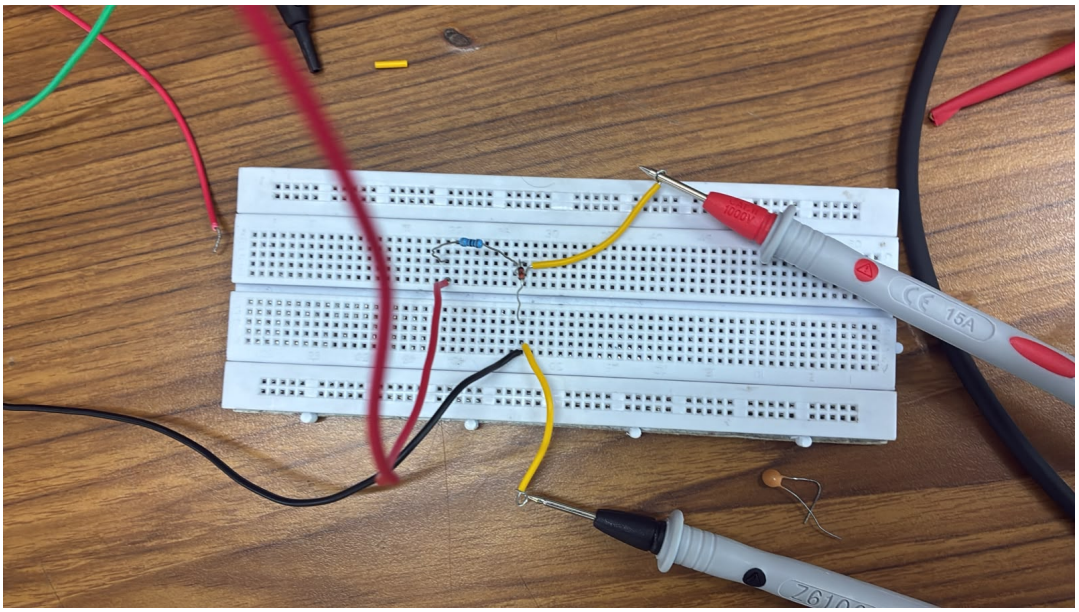


Figure 7: Positive Bias Zener Circuit

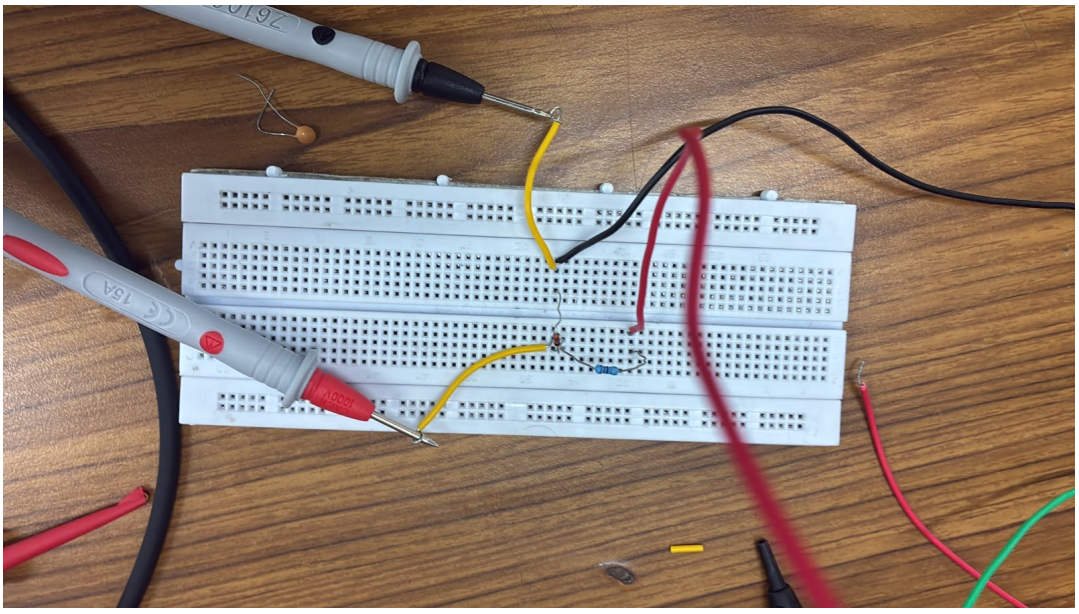


Figure 8: Negative Bias Zener Circuit

4.1 Theory

A Zener diode is a heavily doped PN junction meant to be operated in reverse breakdown without getting damaged. Its forward characteristic is the same as a normal diode. In reverse bias, once the voltage reaches the Zener voltage V_Z, the current increases sharply while the voltage stays almost constant – this near-vertical knee is what makes it useful as a voltage reference. Breakdown below about 5 V is mainly due to the Zener effect (field emission), and above about 6 V it is mainly avalanche multiplication.

The Zener resistance is calculated from the slope of the breakdown region:

$$R_Z = \frac{\Delta V_Z}{\Delta I_Z} \tag{2}$$

4.2 Observations - Forward Bias (to be filled in lab)

This part was not simulated – it will be done directly in the lab with the 1N4733A Zener diode, since the exact breakdown behaviour depends on the physical device and is best measured directly rather than simulated.

4.3 Circuit and Simulation - Forward Bias

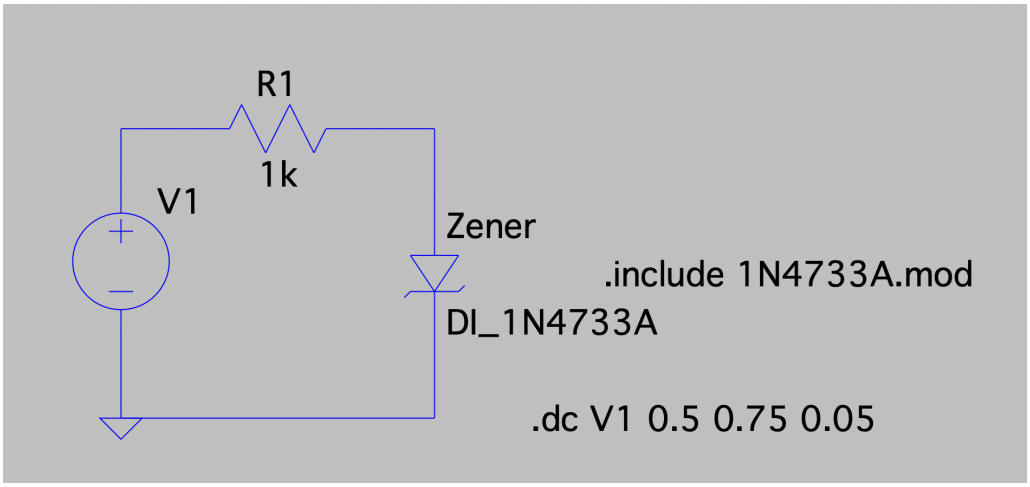


Figure 9: Forward Biased Zener Diode Circuit

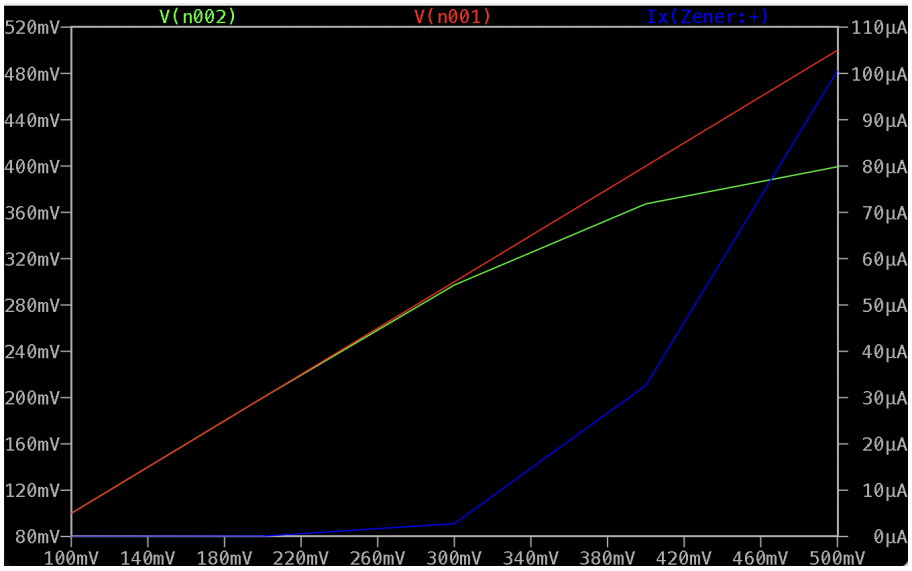


Figure 10: Simulation 1 - LTSpice

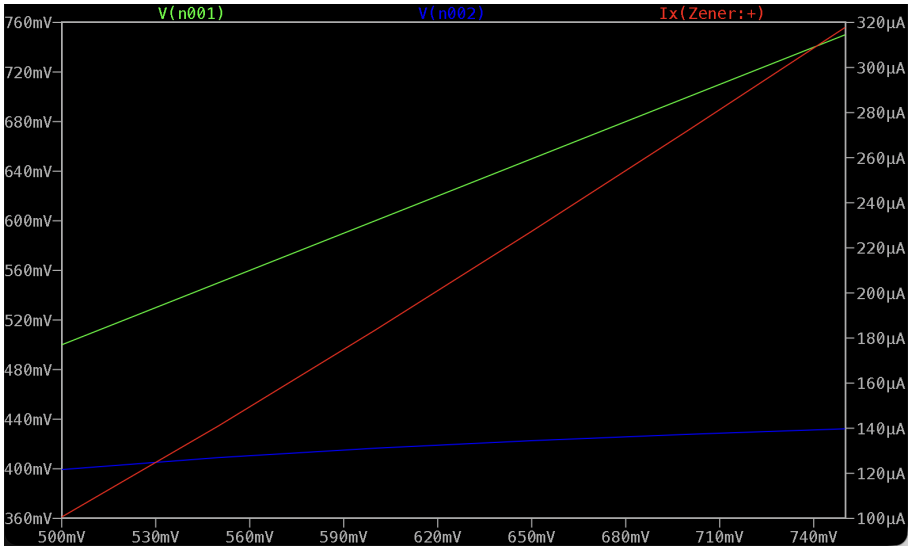


Figure 11: Simulation 2 - LTSpice

Table 3: Zener Diode Forward Bias Characteristics and Source Voltage Measurements

Diode Voltage Vf (V)	**Diode Current (mA)**	**Power Source Voltage (V)**
0	0	0
0.1	0	0.1
0.2	0	0.2
0.3	0	0.3
0.4	0	0.4
0.5	0.0002	0.5
0.548	0.0016	0.55
0.592	0.008	0.6
0.625	0.025	0.65
0.645	0.055	0.7
0.66	0.0915	0.75
0.669	0.1315	0.8
0.676	0.174	0.85
0.717	0.785	1.5
0.73	1.275	2
0.743	2	2.74
0.7604	4.006	4.75
0.7706	5.998	6.74
0.779	8.005	8.74
0.785	9.995	10.7
0.7907	12	12.68
0.794	14.004	14.64
0.797	16.01	16.59
0.801	18	18.53
0.804	20	20.43

From the reverse plot, V_Z and R_Z will be read off from the near-vertical breakdown knee.

4.4 Circuit and Simulation - Reverse Bias

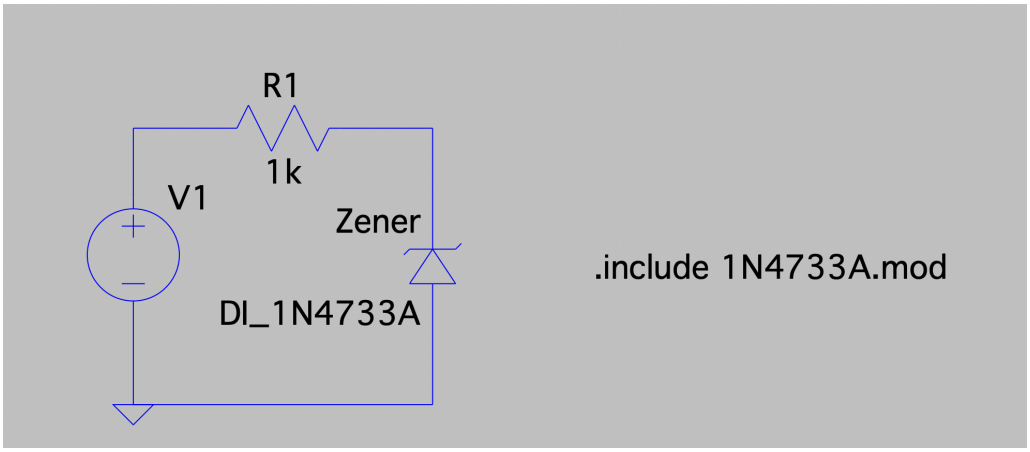


Figure 12: Forward Biased Zener Diode Circuit

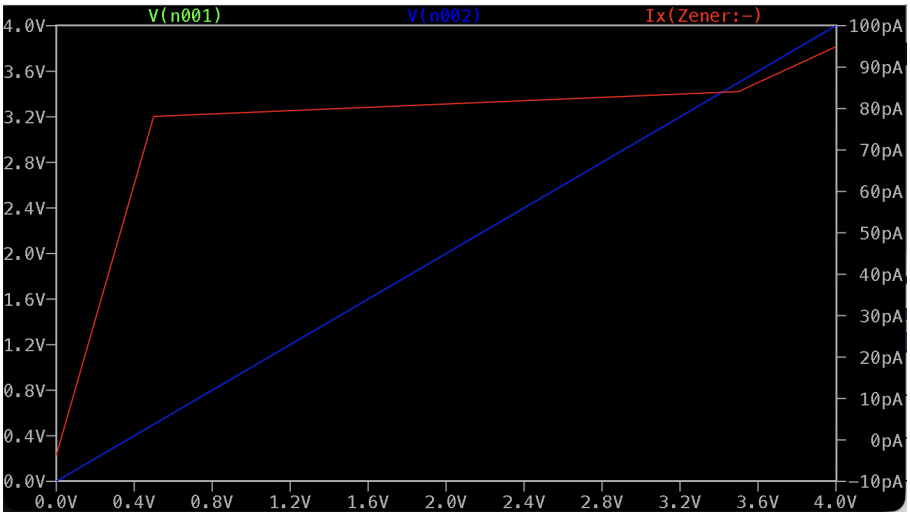


Figure 13: Simulation 1 - LTSpice

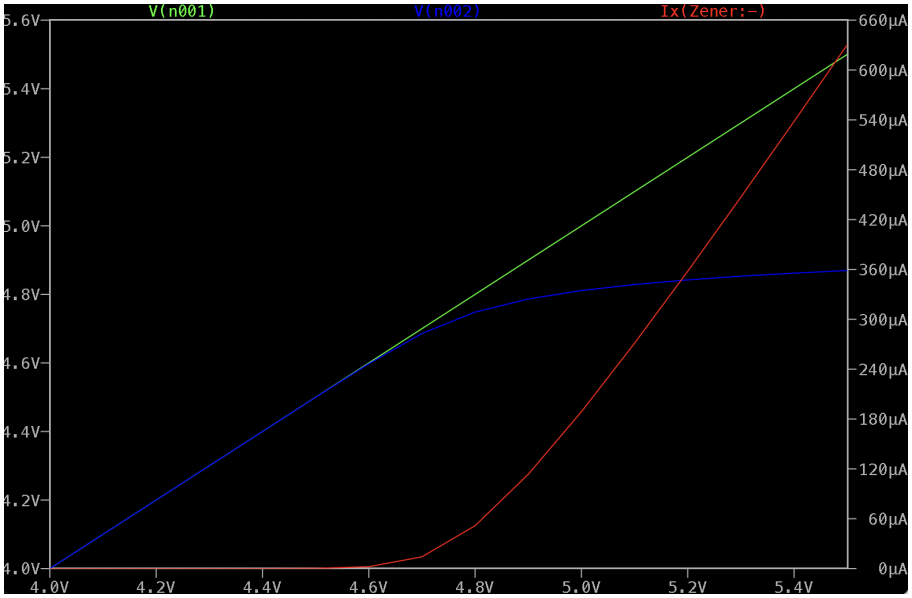


Figure 14: Simulation 2 - LTSpice

4.5 Observations - Reverse Bias (to be filled in lab)

Table 4: Reverse Bias Diode Characteristics and Power Source Voltage Measurements

Diode Voltage Vf (V)	**Current (mA)**	**Power Source Voltage (V)**
0.0006	0	0
0.5	0	0.5
1	0	1
1.5	0	1.5
2	0	2
2.5	0.0005	2.5
3	0.0045	3
3.48	0.022	3.5
3.92	0.079	4
4.003	0.098	4.1
4.08	0.12	4.2
4.1529	0.15	4.3
4.22	0.181	4.4
4.28	0.217	4.5
4.34	0.258	4.6
4.4	0.303	4.7
4.45	0.352	4.8
4.5	0.405	4.9
4.54	0.462	5
4.58	0.523	5.1
4.617	0.587	5.2
4.65	0.655	5.3
4.68	0.725	5.4
4.708	0.797	5.5
4.936	2	6.93
5.06	4	9.05
5.1221	6	11.1
5.155	8	13.1
5.18	10	15.17
5.2	12	17.17
5.2186	14	19.05
5.23	16	21.06
5.241	18	22.96
5.25	20	24.96

5 Clipper Circuits

5.1 Theory

A clipper circuit cuts off part of a waveform above or below some reference level using a diode. Series clippers pass the signal only when the diode conducts; shunt clippers use the diode to short the unwanted part of the signal to a reference level. Clippers are useful for waveform shaping and for protecting circuits from over-voltage.

5.2 Positive Clipper (clips above +1 V)

Here the diode conducts and clamps the output to +1 V whenever the input goes above +1 V. Below that, the diode is off and the output follows the input.

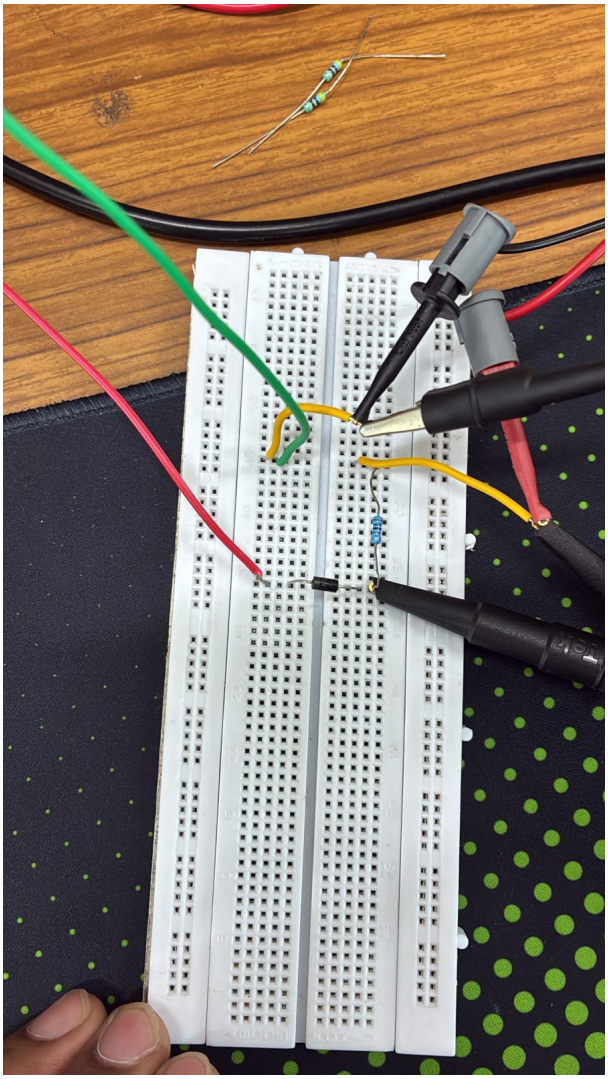


Figure 15: Circuit

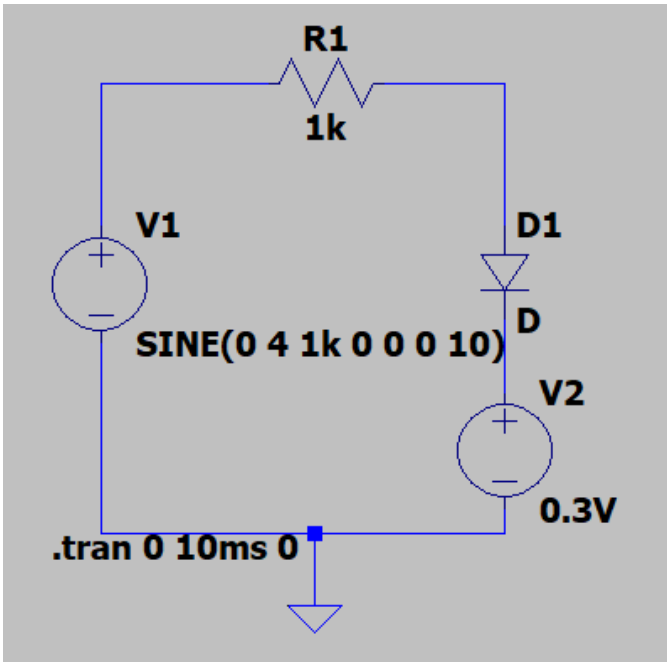


Figure 16: Positive clipper circuit – LTSpice

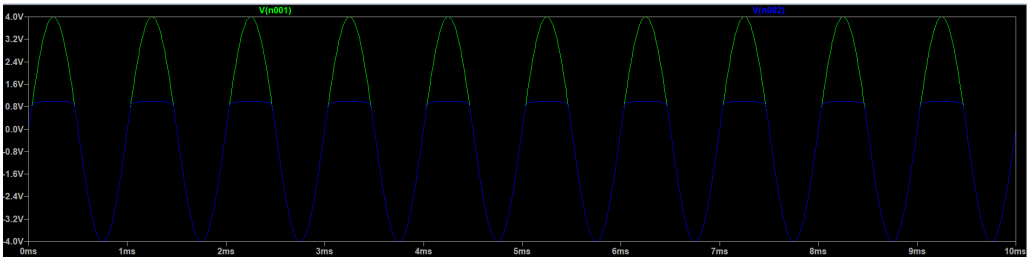


Figure 17: Positive clipper: input and output waveforms

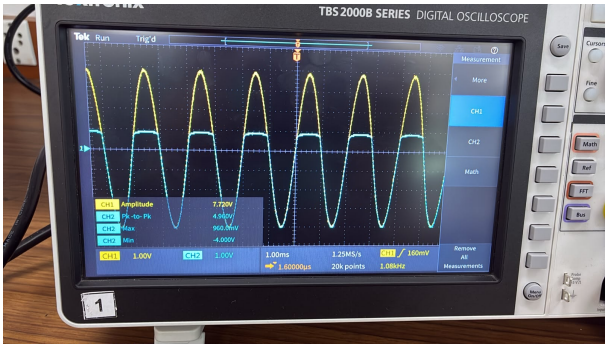


Figure 18: Observed Waveform

The expected clipping level is:

$$V_{out,max} \approx V_{ref} + V_{\gamma} \tag{3}$$

5.3 Negative Clipper (clips below -1 V)

This is the mirror case of the positive clipper – the diode is reversed so the output is clamped whenever the input goes below -1 V.

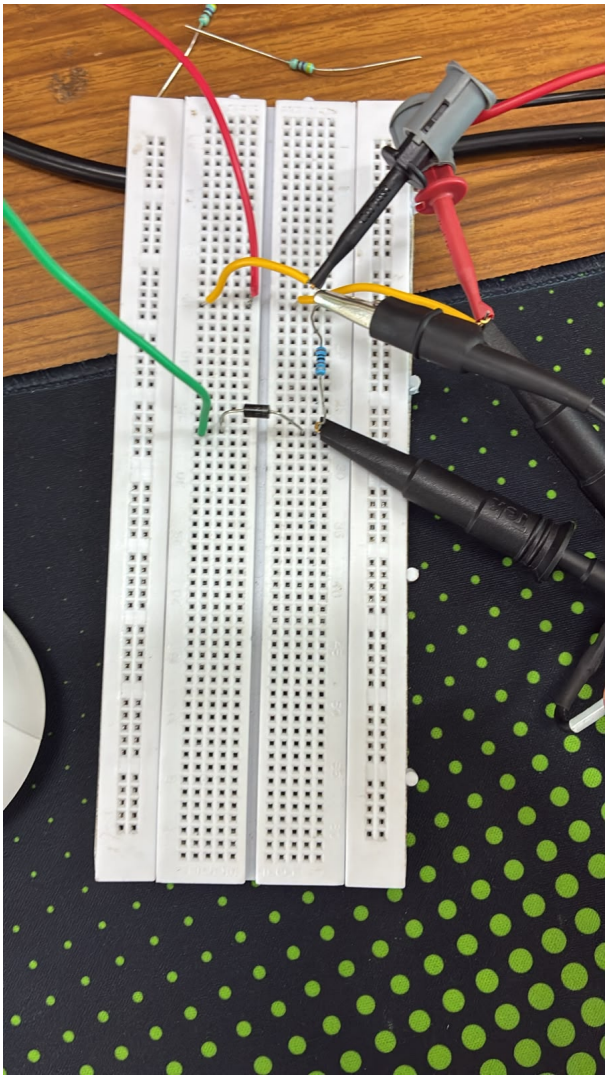


Figure 19: Circuit

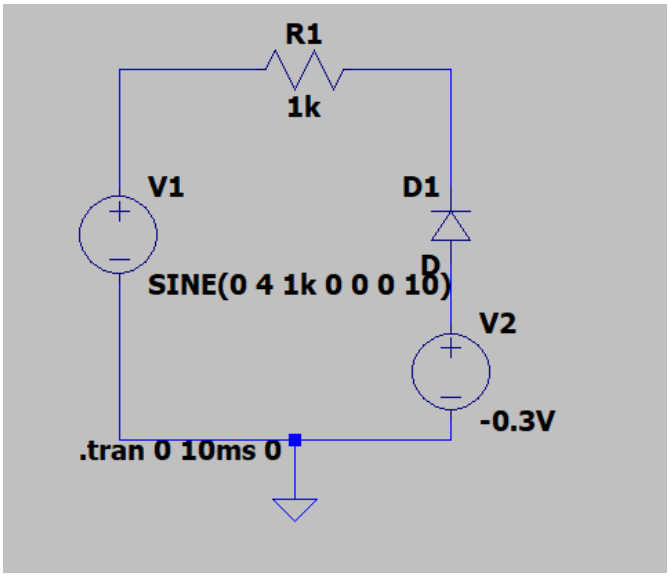


Figure 20: Negative clipper circuit – LTSpice

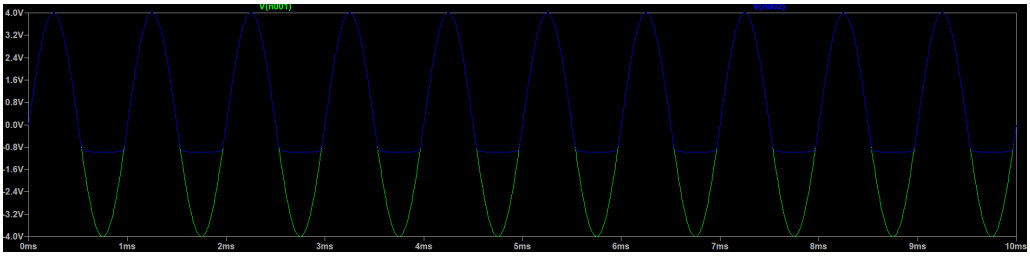


Figure 21: Negative clipper: input and output waveforms

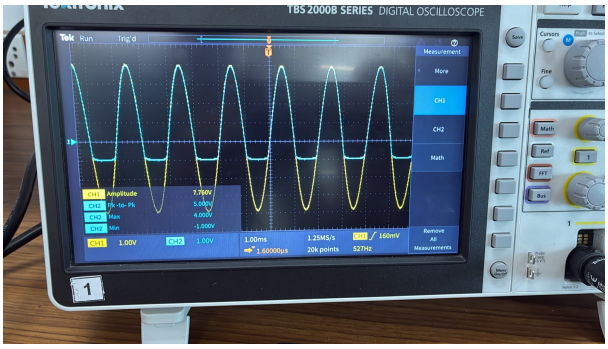


Figure 22: Observed Waveform

5.4 Biased (Two-Level) Clipper

This combines both circuits above at the same output node – one diode referenced to +1 V clips the top of the waveform and the other referenced to −1 V clips the bottom, giving a doubly clipped output.

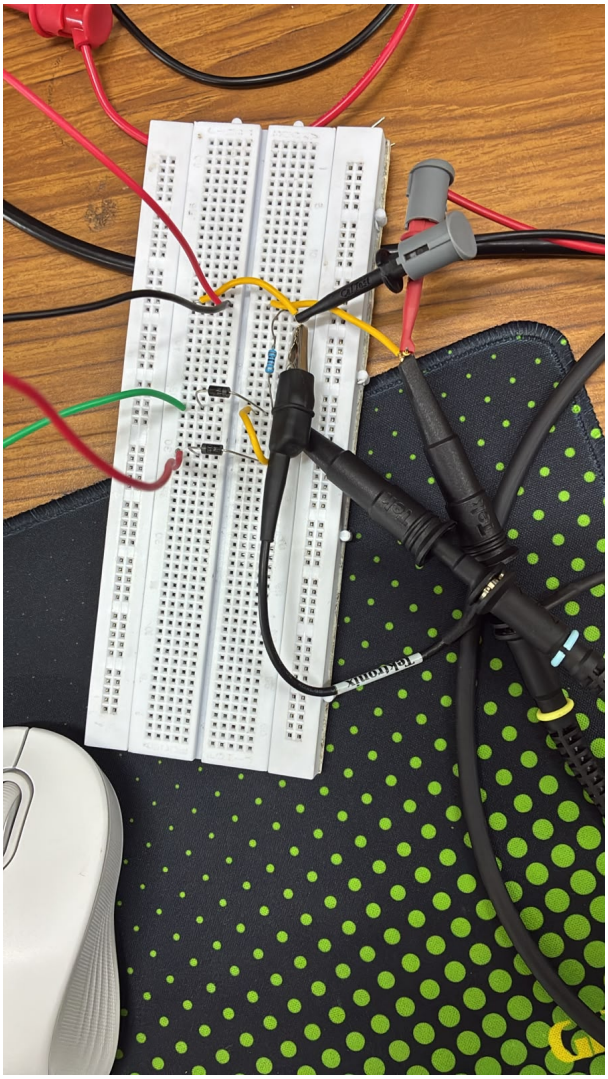


Figure 23: Circuit

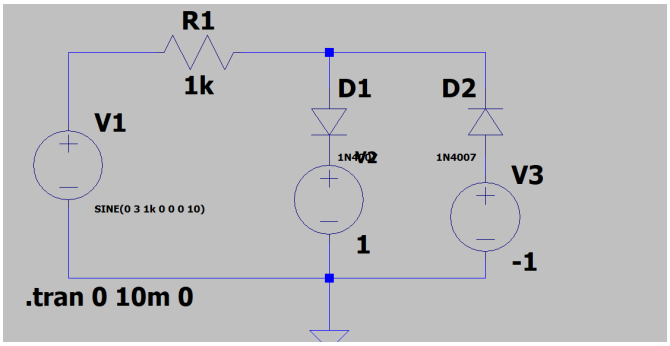


Figure 24: Biased clipper circuit – LTSpice

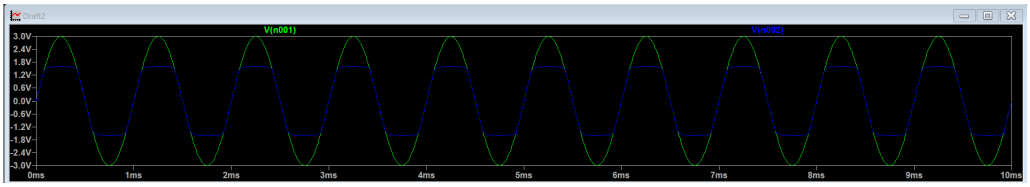


Figure 25: Biased clipper: input and output waveforms, clipped on both sides

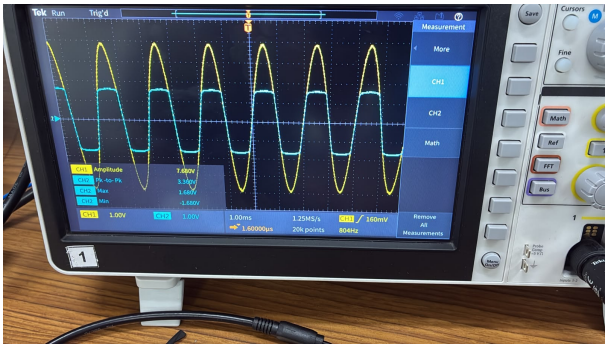


Figure 26: Observed Waveform

5.5 Observation Table – Clippers

Circuit	V_{in} (Vpp)	Reference	V_{out} (measured)	Waveform
Positive clipper	4	+1 V		attached
Negative clipper	4	−1 V		attached
Biased clipper	4	±1 V		attached

6 Clamper Circuits

6.1 Theory

A clamper (DC restorer) shifts a waveform up or down by a fixed amount without changing its shape. It uses a series capacitor and a diode – the capacitor charges up to nearly the peak input voltage during the half cycle when the diode conducts, and this charge then adds a DC offset to the signal for the rest of the cycle.

- **Positive clamper**: shifts the waveform upward, fixing the minimum near a chosen level.
- **Negative clamper**: shifts the waveform downward, fixing the maximum near a chosen level.

The theoretical DC shift is approximately equal to the peak input amplitude minus the diode drop:

$$\Delta V \approx V_{peak} - V_{\gamma} \tag{4}$$

6.2 Positive Clamper

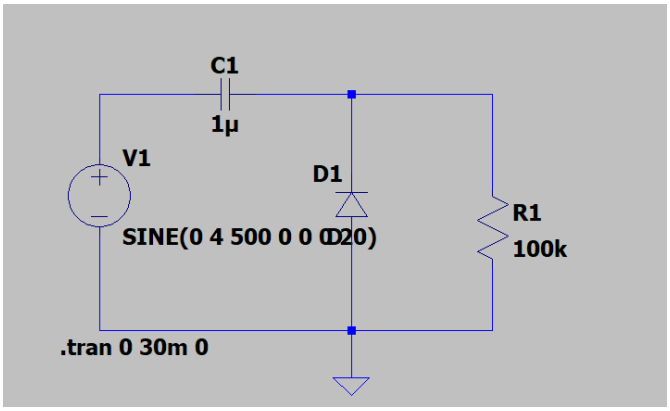


Figure 27: Positive clamper circuit – LTSpice

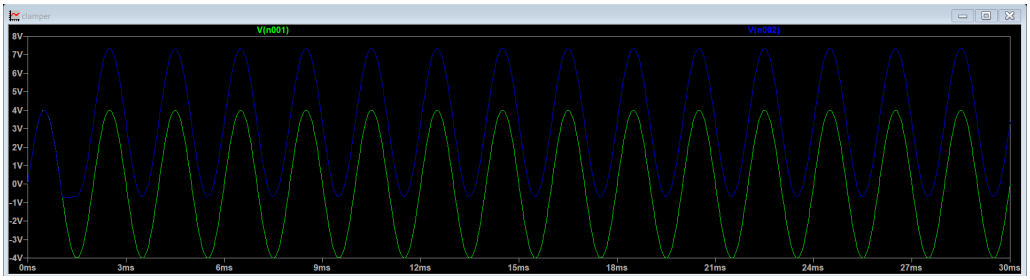


Figure 28: Positive clamper: input and output waveforms, DC level shifted up

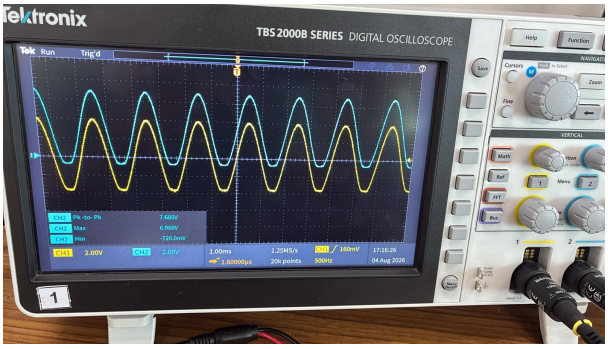


Figure 29: Observed Waveform

6.3 Negative Clamper

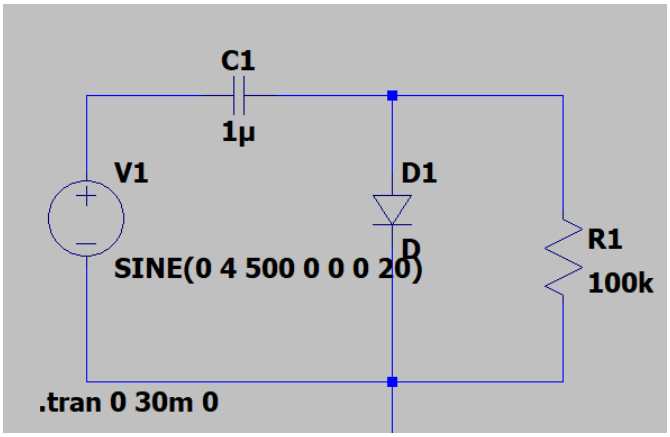


Figure 30: Negative clamper circuit – LTSpice

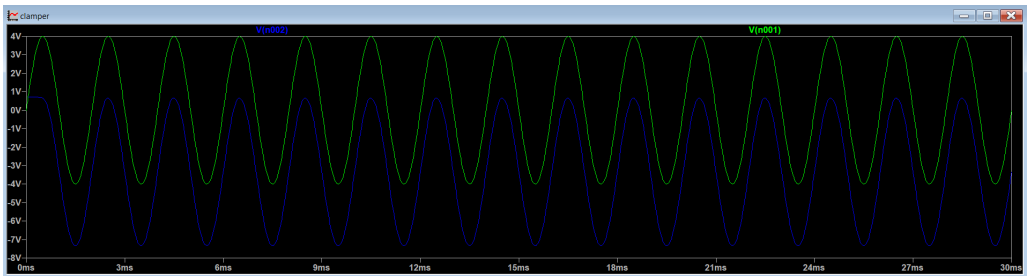


Figure 31: Negative clamper: input and output waveforms, DC level shifted down

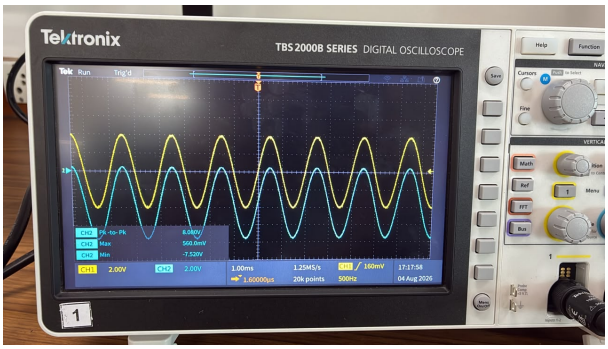


Figure 32: Observed Waveform

6.4 Observation Table – Clampers

Circuit	V_{in} (Vpp)	Expected shift	Measured shift
Positive clamper	4	$\approx V_{peak} - V_{\gamma}$	
Negative clamper	4	$\approx V_{peak} - V_{\gamma}$	

7 Calculations / Analysis

- From the PN diode forward data, the cut-in voltage V_γ will be read off, and static resistance (V/I) and dynamic resistance ($\Delta V/\Delta I$) will be computed near the operating point.
- From the reverse data, the reverse saturation current and breakdown voltage (if seen) will be noted.
- From the Zener data, V_Z and $R_Z = \Delta V_Z/\Delta I_Z$ will be computed from the breakdown region.
- For each clipper, the measured clipping level will be compared with the predicted value $V_{ref} \pm V_\gamma$.
- For each clamper, the measured DC shift will be compared with the theoretical value $\approx V_{peak} - V_\gamma$.

8 Results and Conclusion

The forward V–I characteristic of the PN junction diode was simulated in LTSpice and shows the expected exponential rise in current after the cut-in voltage. The clipper circuits (positive, negative, and biased) correctly clipped the input waveform at the set reference levels, as seen in the simulated input-output plots. The clamper circuits shifted the DC level of the waveform up or down as expected, without changing its shape. The Zener diode characteristics and the reverse-bias PN junction characteristics will be measured directly in the lab and added to the observation tables above, since these depend on the physical device behaviour rather than the simplified LTSpice diode model.